

ECE110


Homework 1

Instructor: Hooman Darabi

Sections covered: Review of ECE10


Total of 7 regular questions, 14 points each. The 5 optional problems have each 5 bonus points. Due: 6PM Friday of week 3.

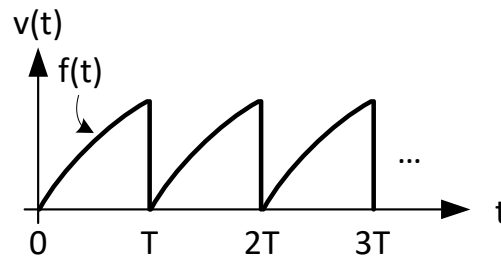1. The voltage waveform below ($v(t)$) is periodic, and is applied to a resistor R . $f(t) = 1 - e^{-t/T}$.
 - a. Plot the energy of the resistor.
 - b. Find the average power dissipated in the resistor in one cycle.




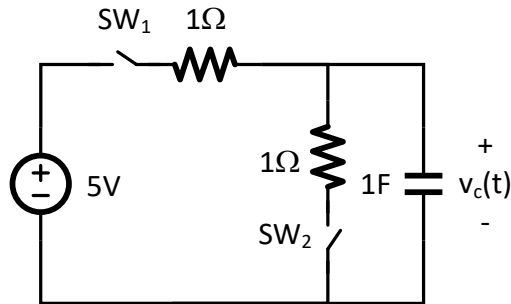2. (Optional) In the circuit below, switch SW_1 is on between 0 and $\frac{T}{2}$, while SW_2 is off, and is off between $\frac{T}{2}$ and T , while SW_2 is on. The pattern repeats. Assume $T = 2S$.
 - a. Plot the capacitor voltage $v_C(t)$ quantitatively.
 - b. Find the steady state values.
 - c. Find the average power delivered to the network by the 5V voltage source when the circuit reaches the steady state.


Hint: Try to replace the source, switches, and resistors with a square-wave voltage source and one series resistance.



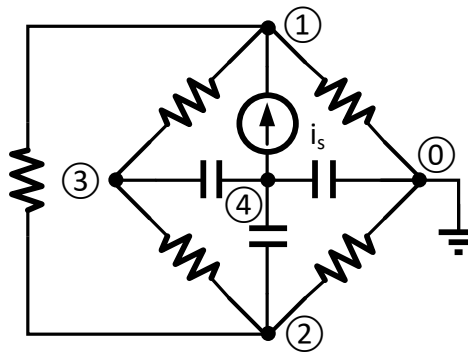3. (Optional) In the network below, the datum node is indicated on the right. Assume all the resistors are 1Ω , and all the capacitors are $1F$. Using node voltage analysis, write the corresponding differential equations (node voltages being the variables, i_s being the input) describing the network. You do not need to solve the equations.




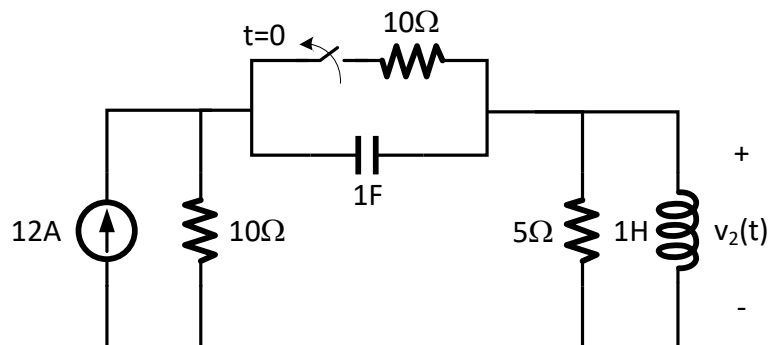4. The circuit below has reached the steady state with the switch closed. At $t = 0$ the switch opens. Find $v_2(0^-)$, $v_2(0^+)$, and $\frac{dv_2}{dt}(0^+)$.




5. Consider the linear and time-invariant circuit below.
- Calculate the zero-input response of the circuit. Express your answer in terms of the capacitor initial voltage ($v_c(0)$).
 - Find the zero-state response if $v(t) = A\cos(\omega t + \varphi)$ by solving the differential equation.

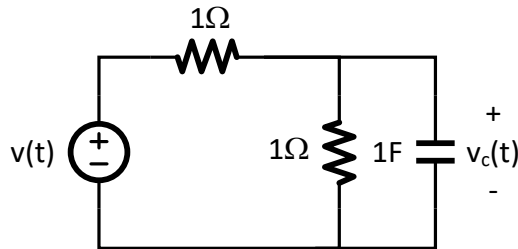
- c. What is the steady-state capacitor voltage?
- d. Redo part c using phasors.
- e. Find the complete response, with $v_C(0) = 1V$, and $v(t) = \cos t$.



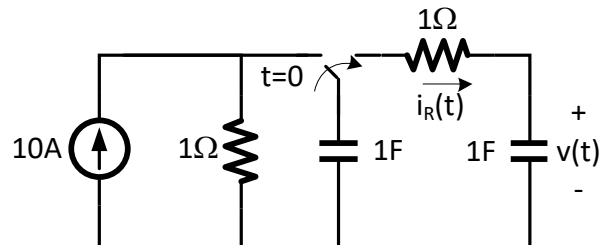6. In the circuit below, the switch has been in the left position for a long time, and is flipped from the left to the right at $t = 0$. Assume $v(0^-) = 0$.
 - a. Determine the order of the circuit (for $t > 0$).
 - b. Find and plot the resistor current. **Hint:** Find $i_R(0^+)$, $i_R(\infty)$, and the time constant by inspection, and use the short-cut method to estimate the 1st-order circuits response. Is the circuit really 1st-order though?
 - c. Find $v(t)$.
 - d. What is the final voltage of the capacitor ($v(\infty)$)? Explain why $v(\infty)$ is not zero, despite the fact that the circuit is in zero-input mode (for $t > 0$).



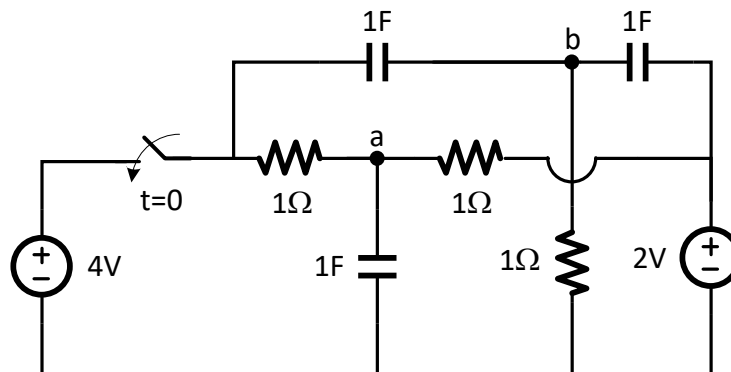7. (Optional) The circuit below has been idle for a long time. At $t = 0$, the switch is closed. Find the voltages $v_a(t)$, $v_b(t)$, and $v_{ab}(t)$. **Hint:** try to break the circuit into two independent (but 1st-order) pieces, and analyze each individually.




8. Find the solution of the following linear differential equations:


a. $y^{(3)} + y = (\cos t)u(t)$, $y(0^-) = 1$, $y'(0^-) = 0$, $y''(0^-) = 0$.

b. $y'' + 2y' + y = \delta(t)$, $y(0) = 0$, $y'(0) = 0$.

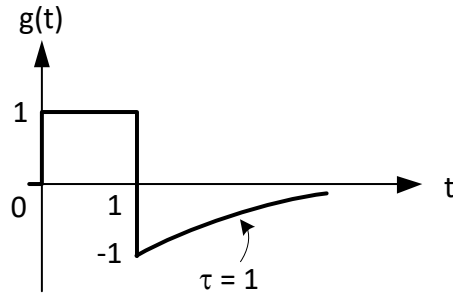c. $y' + 2y = g(t)$, $y(0^-) = 0$, where $g(t)$ is shown below:




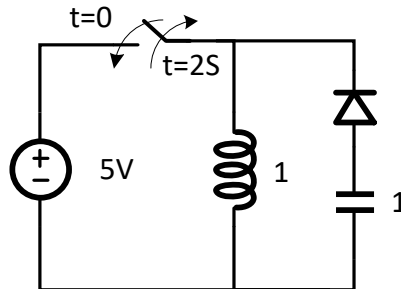9. (Optional) The circuit below is at zero state for $t < 0$. The switch closes at $t = 0$, and opens at $t = 2S$. Find and plot the inductor current and the capacitor voltage. The diode is ideal.



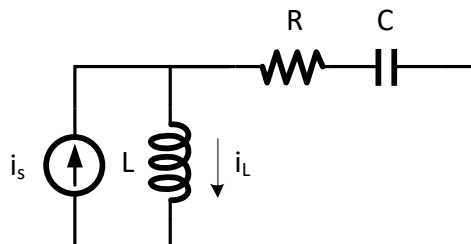10. Given a series RLC circuit (below) with $\omega_0 = 1\text{rad/s}$, $Q = 1/2$,


- Calculate the zero-input response of the circuit (i_L is the output). Express your answer in terms of $i_L(0)$ and $v_C(0)$.
- Find the impulse response by writing and solving the circuit differential equation.
- Intuitively, what are the values of $i_L(0^+)$, and $i_L'(0^+)$?



11. (Optional) The impulse response ($h(t)$) of an LTI circuit is shown on the left.

- Find the step response.

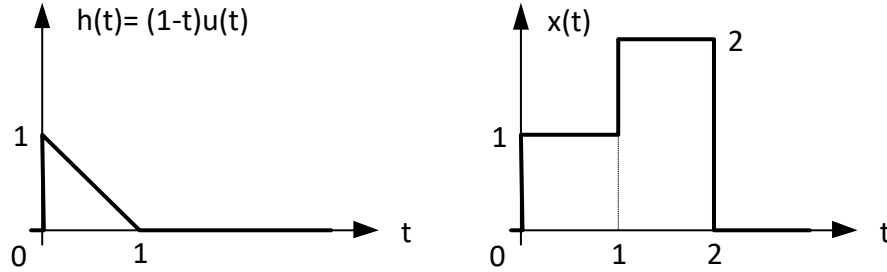- b. Find the response to the input $(x(t))$ shown on the right.



12. The following circuit is in sinusoidal steady state, and $v_s(t) = 2\cos 2t$.

- a. Find the Thevenin equivalent on the left side of nodes ab. **Hint:** Find the open circuit voltage by inspection, and the short circuit current by performing mesh analysis. Show that, $Z_{TH} = M^2 + j(8 - M^2 - \frac{1}{2C_2})$. Note that with $\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$, where I_1 and I_2 are the mesh currents, and A, B, C, D are complex numbers, $I_2 = \frac{-CV_s}{\begin{vmatrix} A & B \\ C & D \end{vmatrix}} = \frac{-CV_s}{AD - BC}$.
- b. Determine the optimum values for M , and C_2 to deliver the maximum power to the load Z_L .

