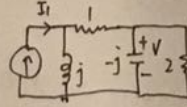


## EE110 Homework 4

Name: Xilai Zhang


UID: 804796478

1. Superposition: when only current source is present,




$$I_1 = e^{j\omega t} \cdot \frac{j}{j + \frac{2-j}{2}} = \frac{2j+1}{3-j}$$


$$V = I_1 \times \frac{-2j}{2-j} = \frac{30+10j}{50}$$

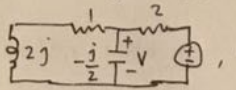thus  $V(t) = 0.63 \sin(t + \arctan(\frac{1}{3}))$ . when only voltage source is present,

$$V = e^{j\omega t} \cdot \frac{\frac{1-0.5j}{1+0.5j}}{2 + \frac{1-0.5j}{1+0.5j}} = \frac{1.75-4j}{15.25}$$

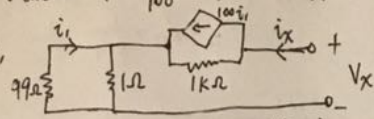, thus  $V(t) = 0.29 \cos(zt + \arctan(-\frac{16}{7}))$ . Theoverall steady voltage across capacitor is the sum of the two,  $V(t) = 0.63 \sin(t + \arctan(\frac{1}{3})) + 0.29 \cos(zt + \arctan(-\frac{16}{7}))$ 2. a.  $V_{th} = 10 \times \frac{1}{100} - 100 \times 0.1 \times 1k = -9999.9$  V. To find  $R_{th}$ , we replace voltage source with a short,

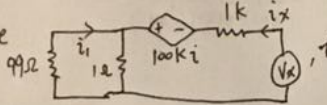and replace dependent current source with dependent voltage source




$$i_x = -100 i_1, V_x = 99 i_1 - 100 k i_1 - 1 k i_x, R_{TH} = \frac{V_x}{i_x} = 0.99 + 2k = 2000.99 \Omega$$

the thevin equivalent is  $-9999.9$  V  $2000.99 \Omega$   $2600 i + 100 i^3$ b.  $-9999.9 = 2000.99 i + 2600 i + 100 i^3$  approximate the equation to  $-10k = 2k i + 2600 i + 100 i^3$ ,we have  $i_1 = -2$ ,  $i_2, i_3 = 1 \pm 7i$ . Thus  $V_1 = -6000$ ,  $V_2 = -12000 - 14000i$ ,  $V_3 = -12000 + 14000i$ .


$$3. \frac{10}{s} \text{ (1+s)} \quad i_{sc} = \frac{10}{s^2} (1+s) \quad R_{norton} = \frac{1}{s+1+\frac{1}{s}} = \frac{s}{s^2+s+1}$$

$$a. \frac{10}{s^2} (1+s) \times \frac{\frac{s}{s^2+s+1}}{\frac{s}{s^2+s+1} + 1} = \frac{10}{s(5+1)} \quad \text{thus } V(t) = (10 - 10e^{-t}) u(t)$$


$$b. \frac{10}{s^2} (1+s) \times \frac{\frac{s}{s^2+s+1}}{\frac{s}{s^2+s+1} + \frac{1}{s}} = \frac{10(1+s)}{s(2s^2+s+1)} \quad \text{thus } V(t) = 10 - 10e^{-\frac{t}{4}} \cos(\frac{\sqrt{7}}{4}t) + e^{-\frac{t}{4}} \frac{10\sqrt{7}}{7} \sin(\frac{\sqrt{7}}{4}t)$$

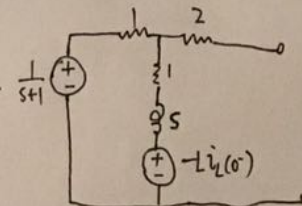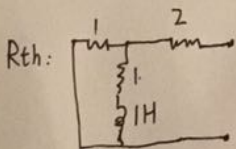4. at steady state,  $V_C(\infty) = 5$  V,  $i_L(\infty) = 5$  A.

$$V_{oc} = (\frac{1}{s+1} + 5) (\frac{1+s}{2+s}) - 5 = \frac{-4}{s+2}$$



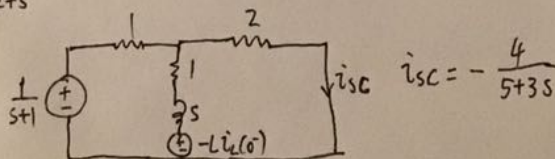
$$R_{th} = 2 + \frac{1+s}{2+s} = \frac{5+3s}{2+s}$$



$$i_{sc} = -\frac{4}{5+3s}$$

a.  $V_c = \frac{-4}{s+2} \times \frac{\frac{1}{s}}{\frac{s+3s}{2+s} + \frac{1}{s}} = \frac{-4}{3s^2+6s+2}$ ,  $V_c(t) = \frac{2\sqrt{3}}{3} e^{(-1-\frac{\sqrt{3}}{3})t} - \frac{2\sqrt{3}}{3} e^{(\frac{\sqrt{3}}{3}-1)t}$

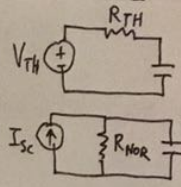b.  $V_c = \frac{-4}{s+3s} \times \frac{\frac{s+3s}{(2+s)s}}{\frac{s+3s}{2+s} + \frac{1}{s}} = \frac{4}{3s^2+6s+2}$ ,  $V_c(t) = \frac{2\sqrt{3}}{3} e^{(-1-\frac{\sqrt{3}}{3})t} - \frac{2\sqrt{3}}{3} e^{(\frac{\sqrt{3}}{3}-1)t}$




6. a.  $-1$  and  $-2$  are natural frequencies of  $V_1$  and  $V_2$ .  
 b. the natural frequencies of the network include  $-1$  and  $-2$ , and could have other natural frequencies.

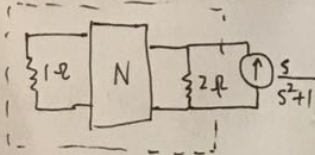c. transform network on the left into  $V_s$  , then the network in

view it as 2-port/

the box is reciprocal. we know  $\begin{cases} V_1 = Z_{11}i_1 + Z_{12}i_2 = 0 \\ V_2 = Z_{21}i_1 + Z_{22}i_2 \end{cases}$ , thus  $\begin{cases} Z_{11} = 1 + \frac{1}{s+1} + \frac{1}{s+2} \\ Z_{21} = Z_{12} = \frac{1}{s+1} - \frac{1}{s+2} \end{cases}$




$$\begin{cases} V_1' = Z_{12}i_2' = (\frac{2}{s+1} - \frac{1}{s+2}) \times (\frac{s}{s^2+1}) = \frac{(s+3)s}{(s+1)(s+2)(s^2+1)} \\ V_2' = Z_{22}i_2' \end{cases}$$

since  $Z_{22}$  is unknown,


$V_2'$  is not known,  $V_1'(t) = \mathcal{L}^{-1}\{V_1'(s)\} = \frac{2}{5}e^{-2t} - e^{-t} + \frac{1}{5}(4\sin t + 3\cos t)$  ~~so the~~ <sup>while so the</sup> steady state

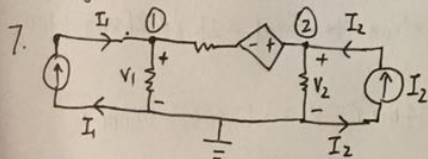voltage  $V_1'(t) = \frac{4}{5}\sin t + \frac{3}{5}\cos t$ .



node analysis:  $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 4.5 & -1 \\ -4 & 2 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$  thus  $y = \begin{bmatrix} 4.5 & -1 \\ -4 & 2 \end{bmatrix}$

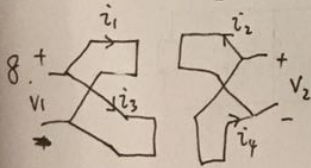and  $Z = y^{-1} = \begin{bmatrix} 0.4 & 0.2 \\ 0.8 & 0.9 \end{bmatrix}$



$$\begin{cases} V_1 = \beta i_2 \\ V_2 = -\beta i_1 \\ V_1 = i_3 R_1 \\ V_2 = (i_4 - 2i_3) R_2 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 + i_3 = \frac{1}{R_1} V_1 - \frac{1}{\beta} V_2 \\ i_2 + i_4 = (\frac{\alpha}{R_1} + \frac{1}{\beta}) V_1 + \frac{1}{R_2} V_2 \end{cases}$$

thus  $y = \begin{bmatrix} \frac{1}{R_1} & -\frac{1}{\beta} \\ \frac{\alpha}{R_1} + \frac{1}{\beta} & \frac{1}{R_2} \end{bmatrix}$