
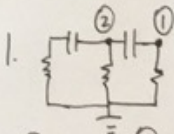


# EE 110 Homework 3


Name: Xilai Zhang VID: 804796478

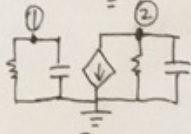


node analysis,  $Y_n = \begin{bmatrix} s+1 & -s \\ -s & 2s+2 \end{bmatrix}$   $\det[Y_n] = s^2 + 4s + 2 = 0$  natural frequencies  $s_{1,2} = -2 \pm \sqrt{2}$



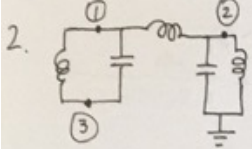
node analysis,  $Y_n = \begin{bmatrix} 1+s & 0 \\ 1 & s+1 \end{bmatrix}$   $\det[Y_n] = s^2 + 2s + 1$  natural frequencies  $s_{1,2} = -1$



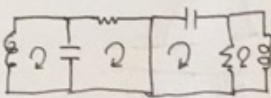node analysis:  $Y_n = \begin{bmatrix} 2s+\frac{2}{s} & -\frac{1}{s} & -2s-\frac{1}{s} \\ -\frac{1}{s} & 2s+\frac{2}{s} & 0 \\ -\frac{1}{s}-2s & 0 & \frac{1}{s}+2s \end{bmatrix}$   $\det[Y_n] = \frac{(2s^2+1)^2}{s^3} = 0$  natural frequencies  $s_{1,2} = \pm \frac{\sqrt{3}}{2}j$   
 $s_{3,4} = -\frac{\sqrt{3}}{2}j$



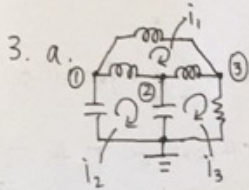mesh analysis:  $Z_b = \begin{bmatrix} s+\frac{1}{s} & -\frac{1}{s} & 0 & 0 \\ -\frac{1}{s} & \frac{1}{s}+1 & 0 & 0 \\ 0 & 0 & \frac{1}{s}+2 & -2 \\ 0 & 0 & -2 & 2+s \end{bmatrix}$   $\det[Z_b] = 2s^2 + \frac{2}{s^2} + 3s + \frac{3}{s} + 5 = 0$   
natural frequencies  $s_1 = -\sqrt{3}$   
 $s_2 = (-1)^{\frac{1}{3}}$   $s_{3,4} = -\frac{1}{4} \pm \frac{\sqrt{3}}{4}j$




mesh analysis:  $\begin{bmatrix} 3s & -s & -s \\ -s & s+\frac{2}{s} & -\frac{1}{s} \\ -s & -\frac{1}{s} & s+\frac{1}{s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} i_1(0^-) - i_2(0^-) - i_3(0^-) \\ i_2(0^-) + V_{C1}(0^-)/s - V_{C2}(0^-)/s \\ i_3(0^-) + V_{C2}(0^-)/s \end{bmatrix}$

node analysis:  $\begin{bmatrix} \frac{2}{s}+s & -\frac{1}{s} & -\frac{1}{s} \\ -\frac{1}{s} & s+\frac{2}{s} & -\frac{1}{s} \\ -\frac{1}{s} & -\frac{1}{s} & 1+\frac{2}{s} \end{bmatrix} \begin{bmatrix} e_1(s) \\ e_2(s) \\ e_3(s) \end{bmatrix} = \begin{bmatrix} -\frac{i_1(0^-)}{s} - \frac{i_2(0^-)}{s} + V_{C1}(0^-) \\ \frac{i_2(0^-)}{s} - \frac{i_3(0^-)}{s} + V_{C2}(0^-) \\ \frac{i_3(0^-)}{s} + \frac{i_1(0^-)}{s} \end{bmatrix}$

b.  $\det[Z_n(s)] = \frac{s(s+1)^2(s^2+3)}{s^2} = 0 \Rightarrow s_{1,2} = -1, s_{3,4} = \pm\sqrt{3}j$

$\det[Y_n(s)] = \frac{(s+1)^2(s^2+3)}{s^2} = 0 \Rightarrow s_{1,2} = -1, s_{3,4} = \pm\sqrt{3}j$  The natural frequencies are the same, also due to inductive loop, there is an extra natural frequency at 0.

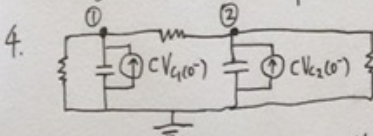c.  $I_1(s) = \frac{I_0 \Delta_{11}}{Z_m(s)} = I_0 \frac{s^4 + s^3 + 3s^2 + 2s + 1}{s(s+1)^2(s^2+3)} \Rightarrow i(t) = \frac{I_0}{s} + k_1 e^{-t} + k_2 t e^{-t} + k_3 \cos(\sqrt{3}t + \phi_3)$  the constant term  $\frac{I_0}{s}$  in the  $i(t)$  expression means that we have a natural frequency at  $s=0$ .



a. node analysis:  $Y_n = \begin{bmatrix} s+2 & -1 \\ -1 & s+2 \end{bmatrix}$   $\det[Y_n] = 0 \Rightarrow s_1 = -1, s_2 = -3$

b.  $e_2(s) = \frac{(s+2)V_{C1}(0^-) + V_{C2}(0^-)}{s^2 + 4s + 3} = \frac{\frac{V_{C1}(0^-) + V_{C2}(0^-)}{2}}{s+1} + \frac{\frac{-V_{C1}(0^-) + V_{C2}(0^-)}{2}}{s+3}$   $e_1(s) = \frac{\frac{V_{C1}(0^-) + V_{C2}(0^-)}{2}}{s+1} + \frac{\frac{V_{C1}(0^-) - V_{C2}(0^-)}{2}}{s+3}$

to eliminate  $s = -1$ , let  $V_{C1}(0^-) = -V_{C2}(0^-)$  would be enough.


c. to eliminate  $s = -3$ , let  $V_{C1}(0^-) = V_{C2}(0^-)$ .  $E = \frac{1}{2} C_1 V_{C1}(0^-)^2 + \frac{1}{2} C_2 V_{C2}(0^-)^2 = 1$  thus  $V_{C1}(0^-) = V_{C2}(0^-) = 1V$

5. a.  $H(s) = \mathcal{L}\{h(t)\} = 1 + \frac{(sta) \cos \phi - w \sin \phi}{(sta)^2 + w^2}$

b.  $H(s) = \mathcal{L}\{h(t)\} = \frac{1}{s+1} - \frac{1}{(s+3)^2} + \frac{2}{s^2}$

c.  $H(s) = \mathcal{L}\{h(t)\} = 1 + s$

Name: Xilai Zhang  
VID: 804796478

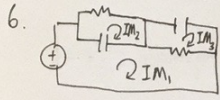


a. mesh analysis 
$$\begin{bmatrix} \frac{1}{C_1 s} + R_2 & -\frac{1}{C_1 s} & -R_2 \\ -\frac{1}{C_1 s} & R_1 + \frac{1}{C_1 s} & 0 \\ -R_2 & 0 & \frac{1}{C_2 s} + R_2 \end{bmatrix} \begin{bmatrix} I_{M_1}(s) \\ I_{M_2}(s) \\ I_{M_3}(s) \end{bmatrix} = \begin{bmatrix} V_1(s) \\ 0 \\ 0 \end{bmatrix}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{C_2 s} I_{M_3}(s)}{I_{M_3}(s)} = \frac{R_1 R_2 C_1 s + R_2}{R_1 R_2 C_1 s + R_2 + R_1 R_2 C_2 s + R_1} = \frac{R_1 R_2 C_1 s + R_2}{(R_1 R_2 C_1 + R_1 R_2 C_2) s + R_1 R_2}$$


zero:  $-\frac{1}{R_1 C_1}$   
pole:  $-\frac{R_1 + R_2}{R_1 R_2 (C_1 + C_2)}$

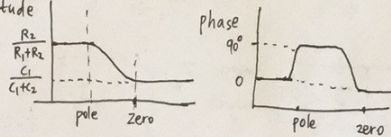b. assume pole is smaller than zero, magnitude



let  $R_1 C_1 = R_2 C_2 = X$ , then

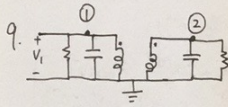c. if  $R_1 C_1 = R_2 C_2$ ,  $G(s) = \frac{X R_2 s + R_2}{X R_2 s + R_2 + X R_1 s + R_1} = \frac{R_2 (Xs + 1)}{(R_1 + R_2)(Xs + 1)} = \frac{R_2}{R_2 + R_1} = \frac{\frac{C_1}{C_2} R_1}{\frac{C_1}{C_2} R_1 + R_1} = \frac{C_1}{C_1 + C_2}$  for all  $s$ .



a.  $L = \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix}$   $\Gamma = L^{-1} = \begin{bmatrix} 1 & -1 \\ -1 & 2 \end{bmatrix}$  node analysis: 
$$\begin{bmatrix} 1 + C_1 s + \frac{1}{R_1 s} & \frac{1}{R_2 s} \\ \frac{1}{R_2 s} & \frac{1}{R_2 s} + C_2 s + 1 \end{bmatrix} \begin{bmatrix} e_1(s) \\ e_2(s) \end{bmatrix} = \begin{bmatrix} I_1(s) \\ 0 \end{bmatrix}$$

$$e_1(s) = \left( \frac{2}{s} + s + 1 \right) I_1(s) \times \frac{s^2}{s^4 + 2s^3 + 4s^2 + 3s + 1}$$
 
$$\frac{V_1(s)}{I_1(s)} = \frac{s^3 + s^2 + 2s}{s^4 + 2s^3 + 4s^2 + 3s + 1}$$

b. similarly,  $\frac{V_2(s)}{I_1(s)} = \frac{e_2(s)}{I_1(s)} = \frac{s}{s^4 + 2s^3 + 4s^2 + 3s + 1}$

c. from a and b,  $\frac{e_2(s)}{e_1(s)} = \frac{V_2(s)}{V_1(s)} = \frac{s}{s^3 + s^2 + 2s}$



Xilai Zhang 804796478

10.


a. suppose we have a voltage source  $\begin{array}{c} + \\ \text{V} \\ - \end{array} \parallel N$ , then when calculating network function we replace it with a short  $\begin{array}{c} \text{ } \\ \text{ } \\ \text{ } \end{array} \parallel N$ , and the pole of the network function won't change, it is equivalent to  $\begin{array}{c} + \\ \text{V} \\ - \end{array} \parallel N$ , where the voltage source becomes an initial state of the network.

b. suppose we have a current source  $\begin{array}{c} + \\ \text{V}_1 \\ - \end{array} \parallel N$ , then when calculating network function we replace it with open  $\begin{array}{c} + \\ \text{V}_1 \\ - \end{array} \parallel N$ , and pole of network function won't change. We can move this current source into the network  $\begin{array}{c} + \\ \text{V}_1 \\ - \end{array} \parallel N$  and make it an initial condition.

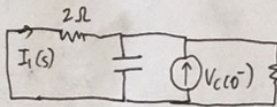c. 
$$Y(s) = \frac{\frac{1}{2}(s+\frac{1}{2})}{\frac{1}{2}(s+\frac{1}{2})} = \frac{1}{s+1}$$
  


$$Z(s) = 2 + \frac{\frac{1}{s} \times 2}{\frac{1}{s} + 2} = \frac{2(1+s)}{s+\frac{1}{2}}$$
  

$$Z(s) \text{ has pole at } s = -\frac{1}{2}. \quad Y(s) \text{ has pole at } -1,$$



$$I_1(s) = -V_c(0^-) \times \frac{\frac{2 \times \frac{1}{s}}{\frac{1}{s} + 2}}{\frac{2 \times \frac{1}{s}}{\frac{1}{s} + 2} + 2} = -\frac{V_c(0^-)}{Z(1+s)}$$

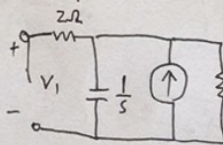Thus the initial state also creates a pole at  $s = -1$  on the short circuit current, and  $i(t) = k e^{-s_1 t}$  is one of the terms.



$$V_1 = V_c(0^-) \times \frac{(\frac{1}{s} \times 2)}{\frac{1}{s} + 2} = \frac{V_c(0^-)}{s+\frac{1}{2}}, \text{ Thus}$$

the initial voltage on capacitor also creates a pole ~~on~~ at  $s = -\frac{1}{2}$  on the open circuit voltage, and  $k e^{-s_2 t}$  would be one of its terms.